

Explanation of S11 and S21 in Spice Simulation

KS Kelvin Kelvin Leung
Created on 4-26-2023
Last Updated on 12-9-2023

Basic of S11 and S21

- Definition of S11 and S21

- $S_{11} = \frac{v_{rev,port1}}{v_{fwd,port1}} = \sqrt{\frac{P_{rev,port1}}{P_{fwd,port1}}}$
 - Given $v_{rev,port2} = 0V$ ($p_{rev,port2} = 0W$)
- $S_{21} = \frac{v_{fwd,port2}}{v_{fwd,port1}} = \sqrt{\frac{P_{fwd,port2}}{P_{fwd,port1}}}$
 - Given $v_{rev,port2} = 0V$ ($p_{rev,port2} = 0W$)

- Remark

- Measurable voltage (v_{rf}) is summation of forward and reverse voltage
 - $v_{rf} = v_{fwd} + v_{rev}$




How to Simulate S21 in Spice with AC Sweep

- Refer to S21 Definition


- $$S_{21} = \frac{v_{fwd,port2}}{v_{fwd,port1}} = \sqrt{\frac{P_{fwd,port2}}{P_{fwd,port1}}}$$
 - Given $v_{rev,port2} = 0$ ($p_{rev,port2} = 0$)

- Simulation Idea

- As no reflection at port 2, system must be terminated by characteristic impedance (50 Ohms)
- As no reflection, direct voltage ($v_{rf,port2}$) measurement at system output equal $v_{fwd,port2}$
 - $v_{rf} = v_{fwd} + v_{rev}$, if $v_{rev} = 0$, $v_{rf} = v_{fwd}$
- If Port 1 is setup to give a forward 1V voltage (i.e. $v_{fwd,port1} = 1V$), AC Sweep voltage at port 2 is S21 as
 - $$S_{21} = \frac{v_{fwd,port2}}{v_{fwd,port1}} = \frac{v_{rf,port2}}{1}$$
- By Port 1 as a 2V voltage source with 50 ohms source impedance, it can guarantee $v_{fwd,port1} = 1V$ in regardless of port 1 loading condition

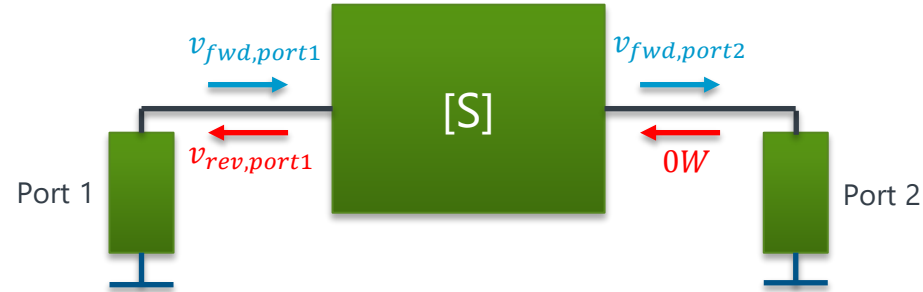


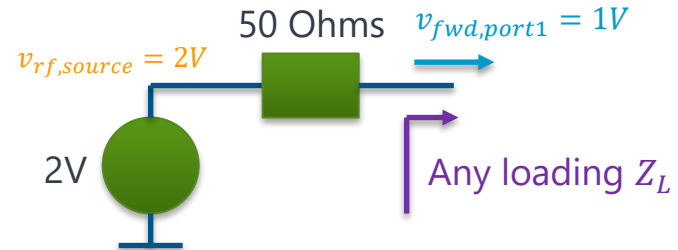Port 1 guarantee to generate 1V forward voltage




How to Simulate S21 in Spice with AC Sweep

- Why this circuit must generate a forward voltage equal half of source voltage
 - In theory, forward voltage is voltage wave travel forward which terminated into characteristic impedance Z_0 (50 ohms)
 - In this circuit, no matter what loading condition is, if we couple forward wave and terminate into 50 ohms, it always
$$v_{fwd,port1} = \frac{v_{rf,source}}{2}$$
 - This is also the reason why signal generator designed to have source impedance equal to characteristic impedance Z_0 , as its voltage or power setpoint can always be equal to forward voltage or forward power

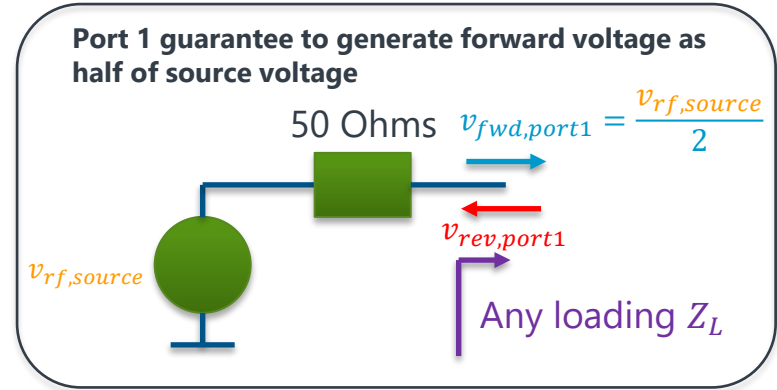


If forward wave is coupled into 50 ohms

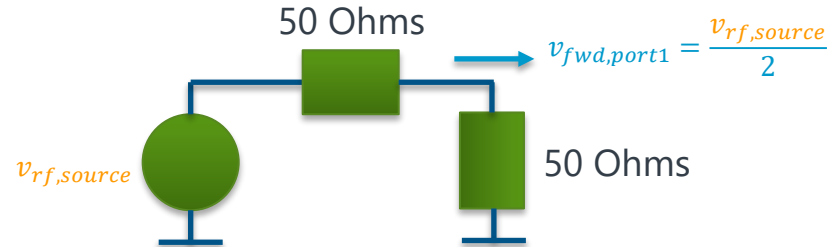


How to Simulate S11 in Spice with AC Sweep

- S_{11} rely on conversion from Z_{11}
 - Z_{11} is impedance measured from port 1 with port 2 terminated at 50ohms
 - If no output from circuit, port 2 not exist and both forward and reverse at port 2 must be 0
 - Z_{11} is a direct measurable parameter in AC Sweep by $Z_{11} = \frac{v_{rf,source}}{i_{rf,source}}$
 - Conversion is $S_{11} = \frac{Z_{11} - Z_0}{Z_{11} + Z_0}$
- A single circuit in Spice to measure both S11 and S21
 - It is possible to use S21 port 1 circuit but measure v_{rf} and i_{rf} after source impedance and calculate $Z_{11} = \frac{v_{rf,x}}{i_{rf,x}}$

Port 1 Circuit to Measure Z11

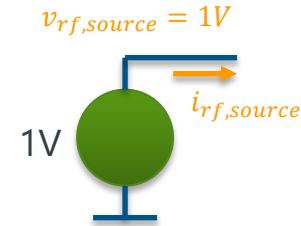

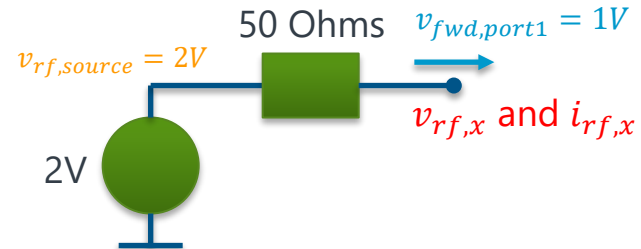
Single Circuit in Spice to Measure S11 and S21




Spice Simulation for S11 and S21

LTSpice Simulation for Z_{11} and S_{21} : LTSpice_Sparam_Simulation.asc

Schematic

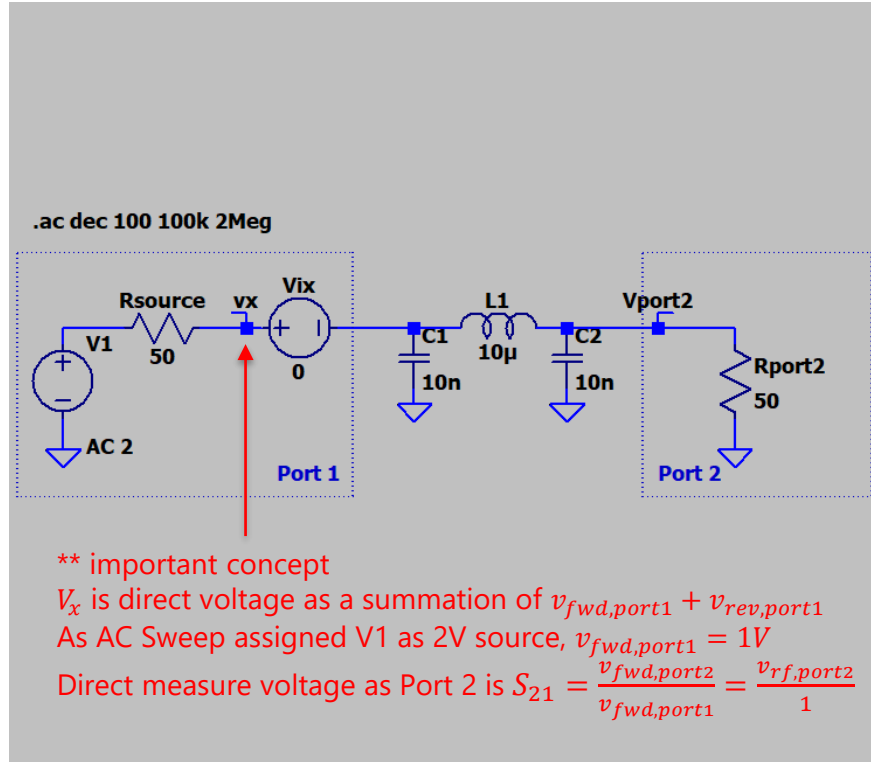


Simulation Result

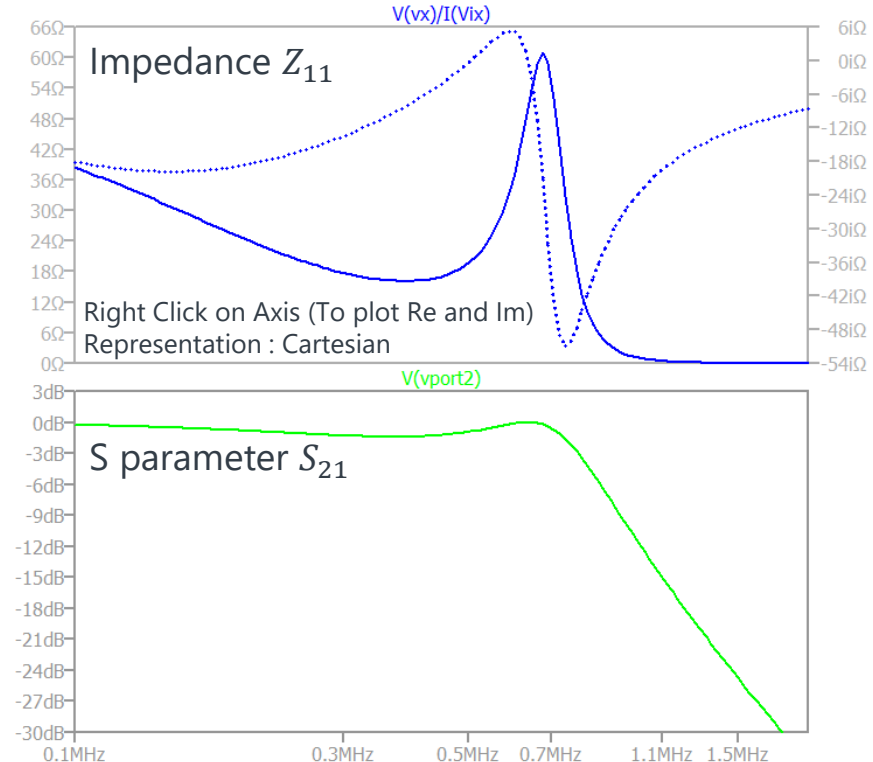

QSpice Simulation for S_{11} and S_{21} : QSpice_Sparam_Simulation.asc

Schematic

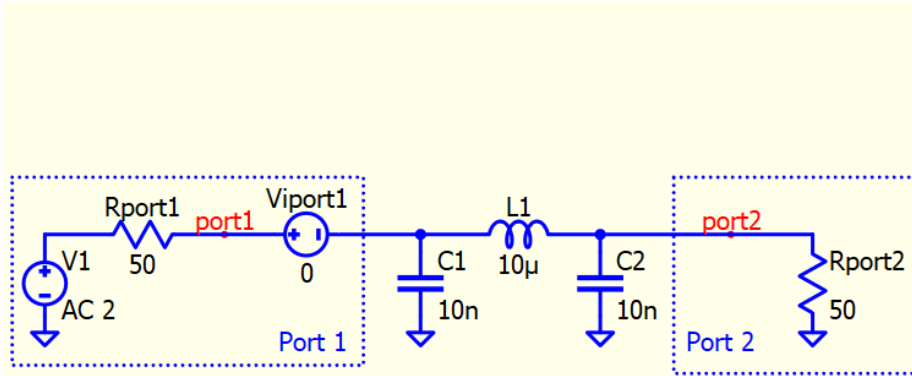

```
.param Zo=50
.func Z11() V(port1)/I(Viport1)
.func S11() (Z11()-Zo)/(Z11()+Zo)
.func S21() V(port2)
.ac dec 100 100K 2Meg
.plot S21()
.plot S11()
```


**** important concept**

$V(\text{port1})$ is direct voltage as a summation of $v_{fwd, \text{port1}} + v_{rev, \text{port1}}$

As AC Sweep assigned V1 as 2V source, $v_{fwd, \text{port1}} = 1V$

Direct measure voltage as Port 2 is $S_{21} = \frac{v_{fwd, \text{port2}}}{v_{fwd, \text{port1}}} = \frac{v_{rf, \text{port2}}}{1}$

Simulation Results

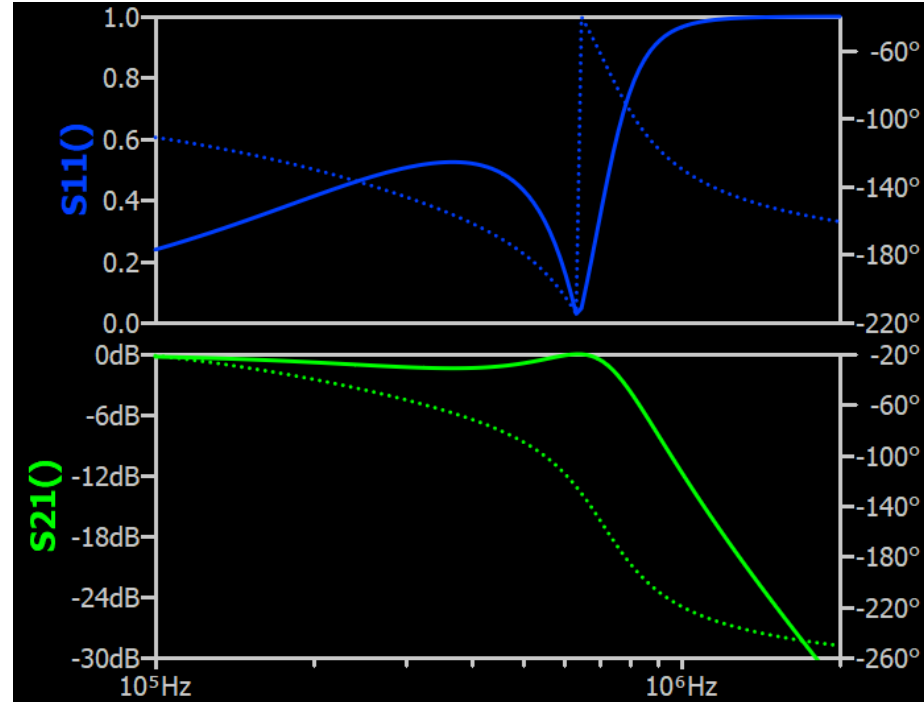

QSpice Simulation for S_{11} and S_{21} : QSpice_Sparam_Simulation.asc

$S_{11}()$ in SmithChart Representation

** Qspice not supports to plot in Cartesian representation yet, it requires post-processing data to plot in SmithChart

Method to plot S_{11} in Microsoft Excel

[1] In Qspice Waveform Viewer, File > Export, Select to export $S_{11}()$ in csv format. Exported S_{11} is in format of $[re(S_{11}), im(S_{11})]$

[2] Rename .csv to .txt, use Excel to import this .txt. In Import Wizard, it will ask for delimiters, select both "Tab" and "Comma"

[3] Use X-Y Scatter plot to plot with x-axis $Re(S_{11})$ and y-axis $Im(S_{11})$

Text Import Wizard - Step 2 of 3

This screen lets you set the delimiters your data contains. You can see how your text is affected in the preview below.

Delimiters

☒ Tab

☐ Semicolon

☒ Comma

☐ Space

☐ Other:

☐ Treat consecutive delimiters as one


Text qualifier: "

Data preview

Frequency	$S_{11}()$	
100000	-0.085738537031553	-0.222103470085669
100300.022396366	-0.0862069839856257	-0.222604649083563
100600.944927116	-0.0866768363854754	-0.223107331730697
100902.770292853	-0.0871480984477546	-0.223611522538355
101205.501202285	-0.0876207744017664	-0.224117226031357


Cancel < Back Next > Finish

Frequency	$S_{11}()$	Real	Imag
100000	-0.08574	-0.2221	
100300	-0.08621	-0.2226	
100600.9	-0.08668	-0.22311	
100902.8	-0.08715	-0.22361	
101205.5	-0.08762	-0.22412	
101509.1	-0.08809	-0.22462	
101813.7	-0.08857	-0.22513	
102119.2	-0.08905	-0.22564	
102425.5	-0.08953	-0.22615	
102732.8	-0.09001	-0.22665	
103041.1	-0.0905	-0.22716	
103350.2	-0.09099	-0.22767	
103660.3	-0.09148	-0.22817	
103971.3	-0.09197	-0.22868	
104283.2	-0.09247	-0.22919	
104596.1	-0.09296	-0.2297	
104909.9	-0.09346	-0.23021	
105224.7	-0.09397	-0.23072	
105540.4	-0.09448	-0.23122	

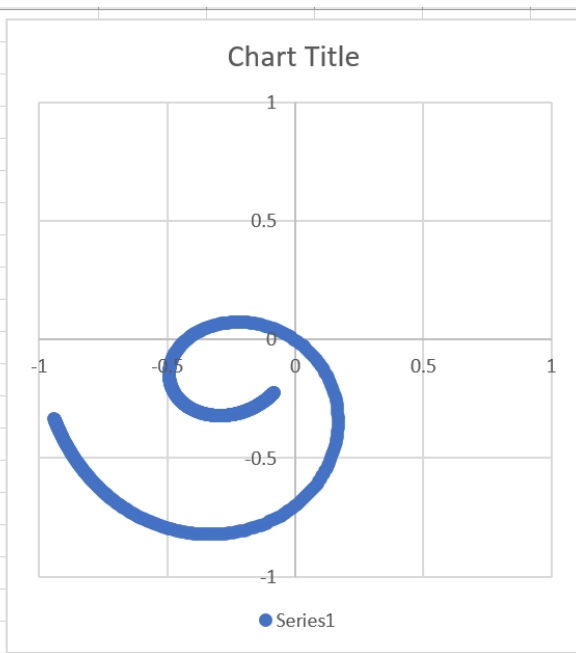


SimNEC Simulation for S_{11} and S_{21} : SimNEC_Sparam_Simulation.ssn


Schematic

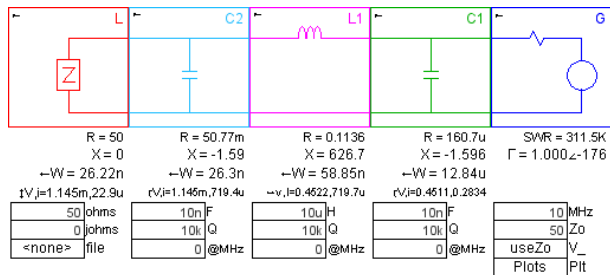

SmithChart S11

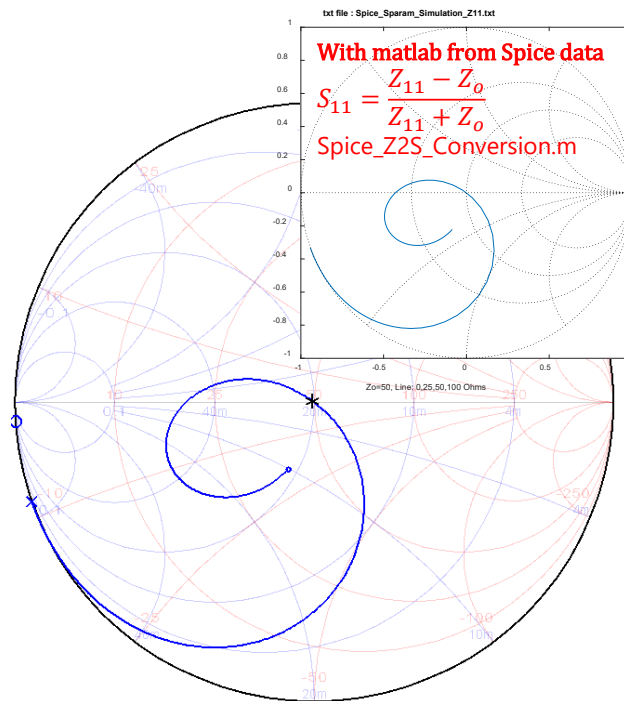

Gain Chart S21

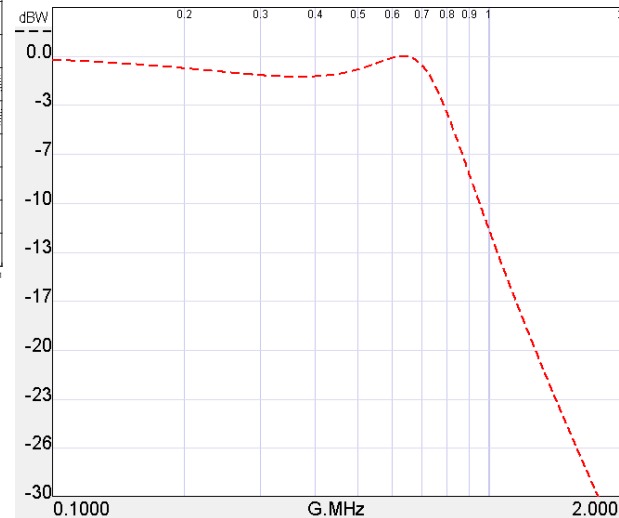

Pwr: [L][C2][L1][G1]